

# Exploring Application-Specific Integrated Circuit (ASIC) for EMT Simulation

Weiping Shi, Texas A&M University  
(wshi@ece.tamu.edu)

Zhenrui Wang, Texas A&M University  
(jerrywang95@tamu.edu)

Karthikeyan Balasubramaniam,  
Argonne National Laboratory  
(kbalasubramaniam@anl.gov)

This work is supported by U.S.  
Department of Energy (DOE)  
Solar Energy Technologies  
Office (SETO), Project #38455.

# Outline


- Overview
- Hardware Accelerator Design
- Circuit Synthesis Results
- Component Design
- Conclusions

# Overview

- Why?
  - Let us look at a real-world example from a different field
  - Etched --- a company founded just two years ago that designs chips for Transformer inference which are 20x faster than NVIDIA H100 GPUs.
  - "Sohu is an order of magnitude faster and cheaper than even NVIDIA's next-generation Blackwell GPUs"
  - And yes, Etched, as the name suggests is an ASIC that implements Transformers at the hardware level – "The world's first transformer ASIC"

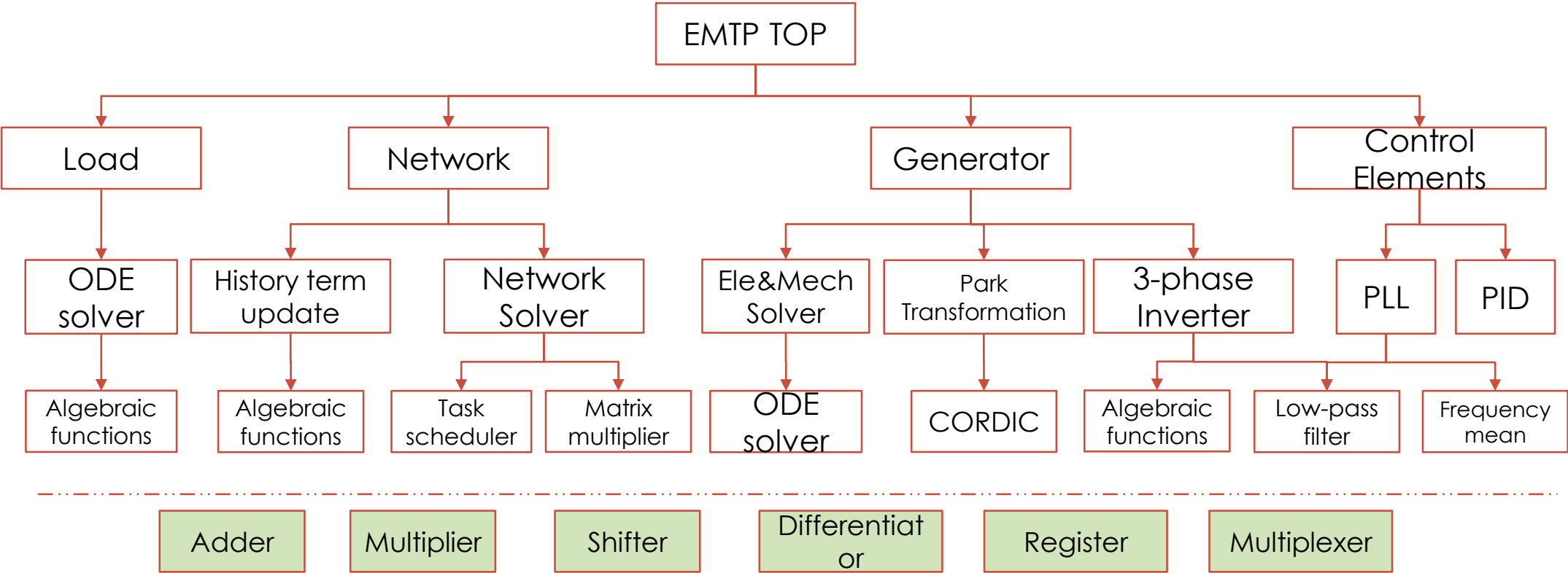
# Overview

- Hardware implementation of the EMT simulation platform
  - Hierarchical structure of the components in the system


 
# Hardware Accelerator Design


- Hardware implementation of the EMT simulation platform
  - Overall hardware architecture



- Dedicated hardware modules for network, generator, loads and control elements
- High speed buses for data transfer between network solver and other elements.
- The Matrix-vector multiplier is the key component in the architecture.
 
# Hardware Accelerator Design

- Design of the Processing Element(PE)
  - The Processing Element(PE) is responsible for dense matrix-vector multiplication of a small tile (e.g. 4x4).
  - We utilize multiple multipliers to conduct the multiplications simultaneously.
  - Results in one row will be summed up through a set of adder tree.




- Hardware cost:
  - 16 multipliers
  - 12 adders
- Delays: 3 cycles

A PE architecture that conduct a 4x4 dense mat-vec ( $y=Ax$ )

 
# Hardware Accelerator Design

- Adaptive matrix multiplier with configurable adder tree



Configurable adder tree architecture


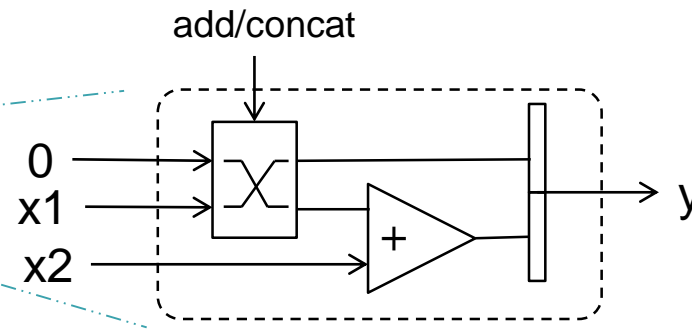
- Each PE is responsible for  $n \times n$  (e.g.  $4 \times 4$ ) dense matvec and produces a vector of length  $n$
- $\oplus$  stands for a configurable unit which act as numerical adder or concatenator





Configurable adder unit
  
# Hardware Accelerator Design

- Mapping the matrix to the architecture
  - Examples of 2 mat-vec of different shapes mapped to the same architecture



  ⊙ Stands for concatenator  
+ Stands for adder





# Hardware Accelerator Design

- Mapping the matrix to the architecture


- Arrange the PEs to form an array

- Assume the total number of PEs is  $2^k$  (k is the number of levels of the tree).
- The possible shape of PE array could be  $(n \cdot 2^r, n \cdot 2^c)$ , where  $r+c=k$ , n is the PE tile size.


- Shaping strategy of the PE array

- **Case 1** (sufficient amount of PEs)

 Shape the PE array so that it covers the whole matrix.



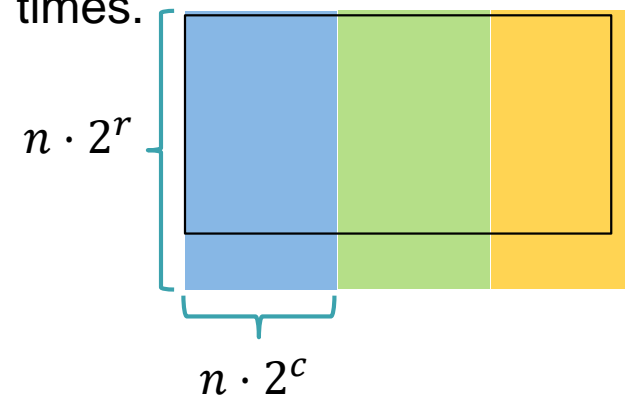- **Case 2** (insufficient amount of PEs)  
Shape the PE array so that it covers part of the columns of the matrix. The whole matrix is covered in multiple times.



# Circuit Synthesis Results

- Circuit synthesis results
  - Synthesis tool: Synopsys Design Compiler
  - **Target library: Nangate open cell library (45nm)**
  - Circuit parameters: Number of PEs: **32**, PE tile size: **8**, Word width: 8 (enough to contain 69-bus system)

➤ Power report

Power Group	Internal Power	Switching Power	Leakage Power	Total Power	( % )
io_pad	0.0000	0.0000	0.0000	0.0000	( 0.00%)
memory	0.0000	0.0000	0.0000	0.0000	( 0.00%)
black_box	0.0000	0.0000	0.0000	0.0000	( 0.00%)
clock_network	2.2662e+04	0.0000	0.0000	2.2662e+04	( 30.58%)
register	5.8182e+03	1.6141e+03	3.3552e+06	1.0788e+04	( 14.56%)
sequential	0.0000	0.0000	0.0000	0.0000	( 0.00%)
combinational	1.7179e+04	1.1350e+04	1.2117e+07	4.0648e+04	( 54.86%)
Total	4.5660e+04 uW	1.2964e+04 uW	1.5472e+07 nW	7.4098e+04 uW	

Power consumption < 0.08 w

➤ Area report

```

Combinational area:          542148.701792
Buf/Inv area:                81716.530028
Noncombinational area:      194482.168945
Macro/Black Box area:       0.000000
Net Interconnect area:      undefined (Wire load has zero net area)

Total cell area:             736630.870737
    
```

Total area < 0.8 mm<sup>2</sup>

# Circuit Synthesis Results

- Circuit performance evaluation

- Based on synthesis result on timing, we can estimate the time needed for the accelerator to solve the 69-bus system
- Circuit parameters: Number of PEs: 32, PE tile size: 8, Word width: 8 (sufficient to process the 69-bus system)

- Timing report

clock clk (rise edge)	10.00	10.00
clock network delay (ideal)	0.00	10.00
tree_genblk1_8__adder_cater_out_reg_0_/CK	0.00	10.00 r
library setup time	-0.04	9.96
data required time		9.96
-----		
data required time		9.96
data arrival time		-1.28
-----		
slack (MET)		8.69


Running frequency > 500Mhz

- Runtime estimation

- Delay for each mat-vec:  $\log 8 + \log 32 + 4 = 12$  cycles.
- To solve the linear system we need 4 mat-vec, thus total delay:  $4 \cdot 12 = 48$  cycles.
- Assume running frequency 500 MHz, total runtime would be  $48 \cdot 2 \text{ ns} = 96 \text{ ns}$ .
- Compared to previous software approach ( $\sim 10 \text{ us}$ ), hardware accelerator gains around 104 times speedup for the 69-bus system.

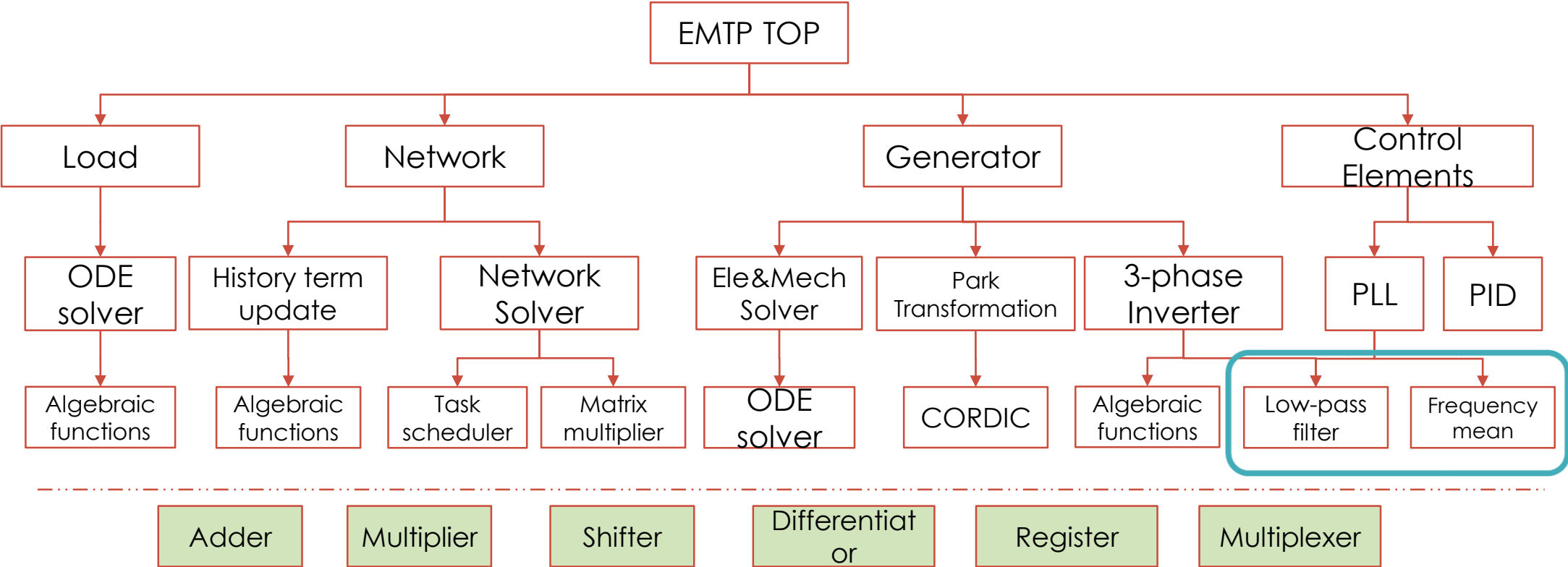
# Component Design

- Hardware implementation of the EMT simulation platform
  - Hierarchical structure of the components in the system


 
# PLL Design -- Variable Frequency Mean Function

- Hardware implementation of the variable frequency mean function




- The variable frequency mean function calculate the mean value of the input signal over a single cycle.

$$\bar{V}(t) = \frac{1}{T} \int_{t-T}^t V(t) \cdot dt$$
 
# PLL Design -- Variable Frequency Mean Function

- Hardware implementation of the variable frequency mean function
  - The running mean form can be implemented very efficiently with minimum hardware requirement.



- 2 multiplier
- 1 adder
- 1 register

# PLL Design -- Low-Pass Filter

- Hardware implementation of the low-pass filter
  - The low-pass filter can remove high-frequency noises thus makes the output frequency smoother and more robust.
  - The general form of the low-pass filter can be expressed as:

$$f'' + 2\xi\omega_n \cdot f' + \omega_n \cdot f = f(t)$$


- To facilitate hardware implementation, we rewrite the equation as:

$$f = \frac{f(t)}{2\pi} - \frac{f''}{\omega_n^2} - \frac{2\xi f'}{\omega_n} = A \cdot f(t) - B \cdot f' - C \cdot f''$$

Now we only need to calculate the derivative and second-order derivative of  $f$ , which can be easily obtained by the difference between current value and history values.
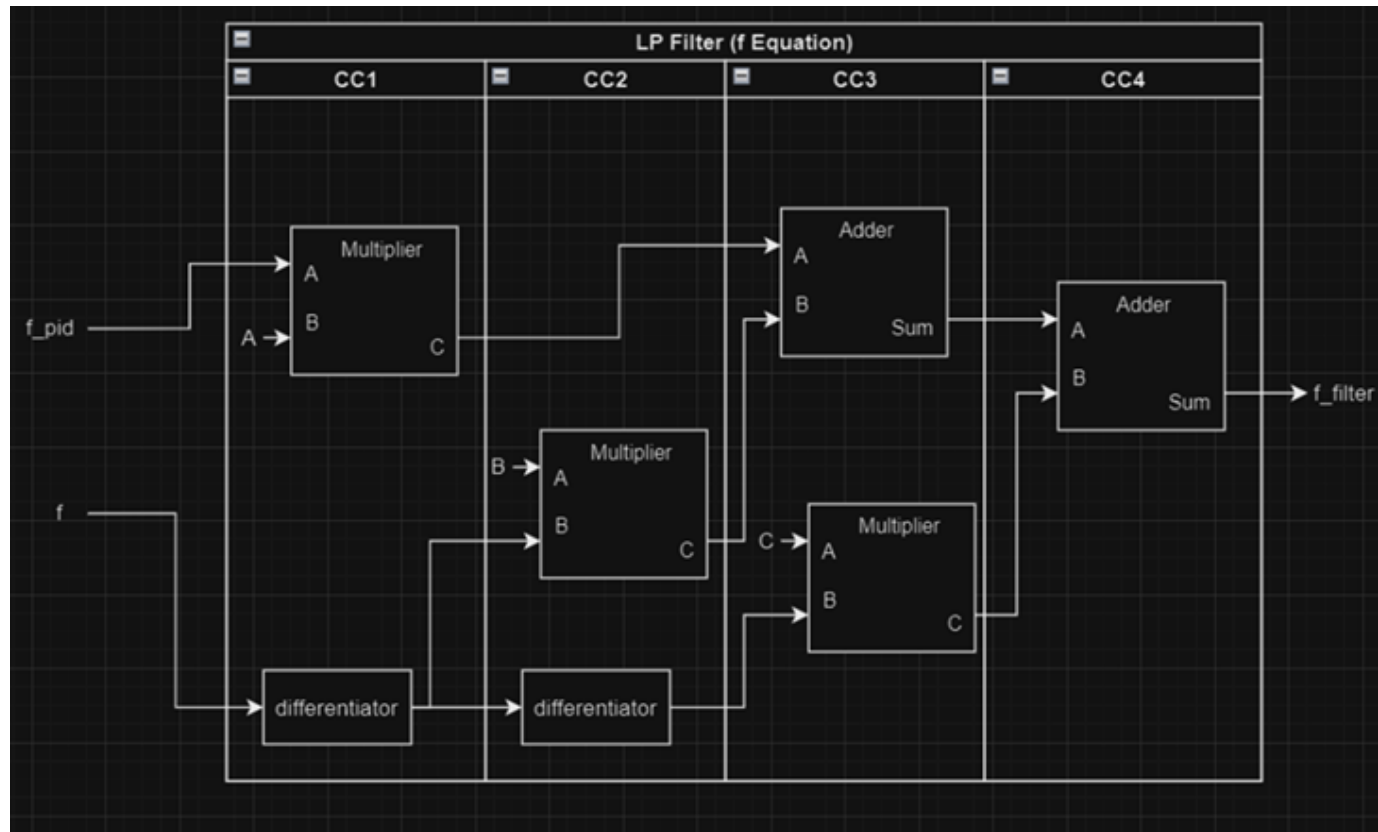
# PLL Design -- Low-Pass Filter

- Hardware implementation of the low-pass filter
  - The design that maximize hardware reuse



Hardware count

- Multiplier: 1
- Adder: 1
- Differentiator: 1
  - Adder: 0 (will use available adders)
  - Shifter: 1
  - Register: 2

Timing

- 4 Cycles
- 1 cycle has delay of 1 multiplier

Another option of the same circuit performs CC3 and CC4 in one cycle.

- Increases hardware usage
- Decreases #CCs



# Conclusions

- ASIC for EMT research is complementary to existing EMT research.
- The research in this space is currently in early stage but has tremendous potential for accelerating EMT studies, drawing inspiration from success stories in other fields.

Questions?